

Computer Architecture Experiment

Lab2



Topics

- 0、 Lab introduction
- Lab 1). Warmup Run you multiple-cycle CPU on 3E board. Try to add one new branch instruction.
- Lab 2). 5-stage pipelined CPU with 15 MIPS instructions (only required to execute in pipeline).
- Lab 3). Implementing "stall" when have hazards
- Lab 4). Implementing "forwarding paths"
- Lab 5). The whole CPU with 31 instructions.

Outline

- Experiment Purpose
- Experiment Task
- Basic Principle
- Operating Procedures
- Precaution

Experiment Purpose 1

- Understand the principles of MC CPU Controller and datapath and master methods of MC CPU Controller and datapath design.
- Understand the principles of Datapath and master methods of Datapath design
- Understand the principles of MC CPU and master methods of MC CPU design
- master methods of program verification of CPU

Experiment Purpose 2

- Understand the principles of Pipelined CPU
- Understand the basic units of Pipelined CPU
- Understand the working flow of 5-stages
- Master the method of simple Pipelined CPU
- master methods of program verification of simple Pipelined CPU

Experiment Task 1

- Design the **CPU Controller, Datapath, bring together** the basic units into Multiple-cycle CPU
- **Verify the MC CPU with program** and observe the execution of program


Experiment Task 2

- Design the **CPU Controller**, and the **Datapath of 5-stages Pipelined CPU**
 - 5 Stages
 - Register File
 - Memory (Instruction and Data)
 - other basic units
- **Verify the Pipelined CPU with program** and observe the execution of program

15 common used MIPS instructions

MIPS Instructions							Operations
Bit #	[31..26]	[25..21]	[20..16]	[15..11]	[10..06]	[05..00]	
R-type	op	rs	rt	rd	sa	func	
add	000000	rs	rt	rd	00000	100000	rd \leftarrow rs + rt; PC \leftarrow PC + 4
sub	000000	rs	rt	rd	00000	100010	rd \leftarrow rs - rt; PC \leftarrow PC + 4
and	000000	rs	rt	rd	00000	100100	rd \leftarrow rs & rt; PC \leftarrow PC + 4
or	000000	rs	rt	rd	00000	100101	rd \leftarrow rs rt; PC \leftarrow PC + 4
sll	000000	00000	rt	rd	sa	000000	rd \leftarrow rt << sa; PC \leftarrow PC + 4
srl	000000	00000	rt	rd	sa	000010	rd \leftarrow rt >> sa (logical); PC \leftarrow PC + 4
sra	000000	00000	rt	rd	sa	000011	rd \leftarrow rt >> sa (arithmetic); PC \leftarrow PC + 4
I-type	op	rs	rt	immediate			
addi	001000	rs	rt	immediate			rt \leftarrow rs + (sign_extend)immediate; PC \leftarrow PC + 4
andi	001100	rs	rt	immediate			rt \leftarrow rs & (zero_extend)immediate; PC \leftarrow PC + 4
ori	001101	rs	rt	immediate			rt \leftarrow rs (zero_extend)immediate; PC \leftarrow PC + 4
lw	100011	rs	rt	immediate			rt \leftarrow memory[rs + (sign_extend)immediate]; PC \leftarrow PC + 4
sw	101011	rs	rt	immediate			memory[rs + (sign_extend)immediate] \leftarrow rt; PC \leftarrow PC + 4
beq	000100	rs	rt	immediate			if (rs == rt) PC \leftarrow PC + 4 + (sign_extend)immediate<<2; else PC \leftarrow PC + 4
bne	000101	rs	rt	immediate			if (rs != rt) PC \leftarrow PC + 4 + (sign_extend)immediate<<2; else PC \leftarrow PC + 4
J-type	op	address					
j	000010	address					PC \leftarrow (PC+4)[31..28],address<<2


Step1: CPU Controller

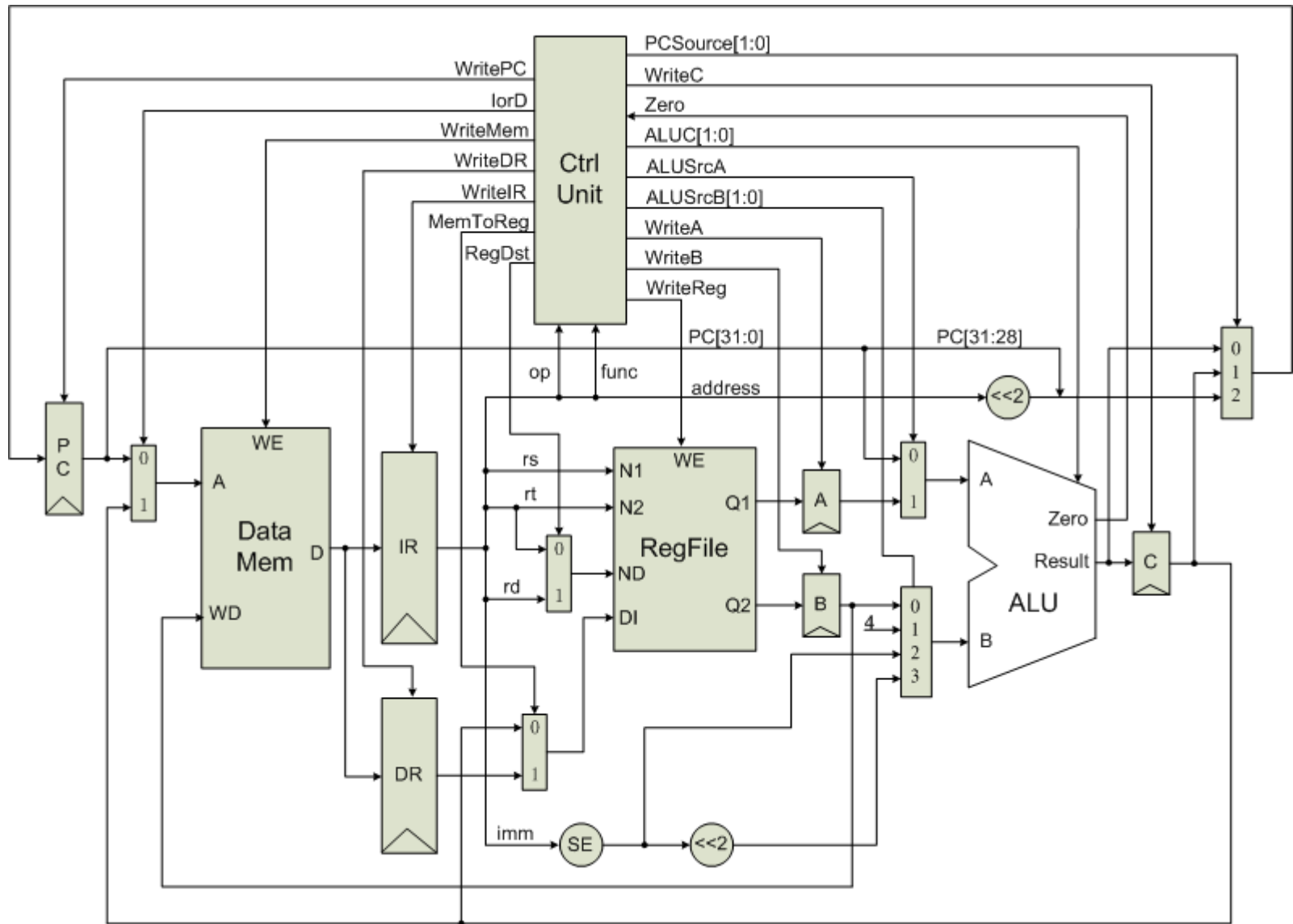

Output of CPU Controller


	Output Signal	Meaning When 1	Meaning When 0
1	PCSrc[1:0]	00: PC + 4;01: Branch Instr.;10: jump Instr	
2	WritePC	Write PC	Not Write PC
3	IorD	Instruction Addr	Data Addr.
4	WriteMem	Write Mem.	Not Write Mem.
5	Write DR	Write Data. Reg	Not Write Data. Reg
6	Write IR	Write Instr. Reg	Not Write Instr. Reg
7	MemToReg	From Mem. To Reg	From ALUOut To Reg
8	RegDest	rd	rt
9	ALUC	ALU Controller Op	
10	ALUSrcA	Register rs	PC
11	ALUSrcB	Selection:00:Reg rt; 01:4; 10:Imm.; 11: branch Address	
12	WriteA	Write A Reg.	Not Write A Reg.
13	WriteB	Write B Reg.	Not Write B Reg.
14	WriteC	Write C Reg.	Not Write C Reg.
15	WriteReg	Write Reg.	Not Write Reg.

The principle of CPU Controller(1)

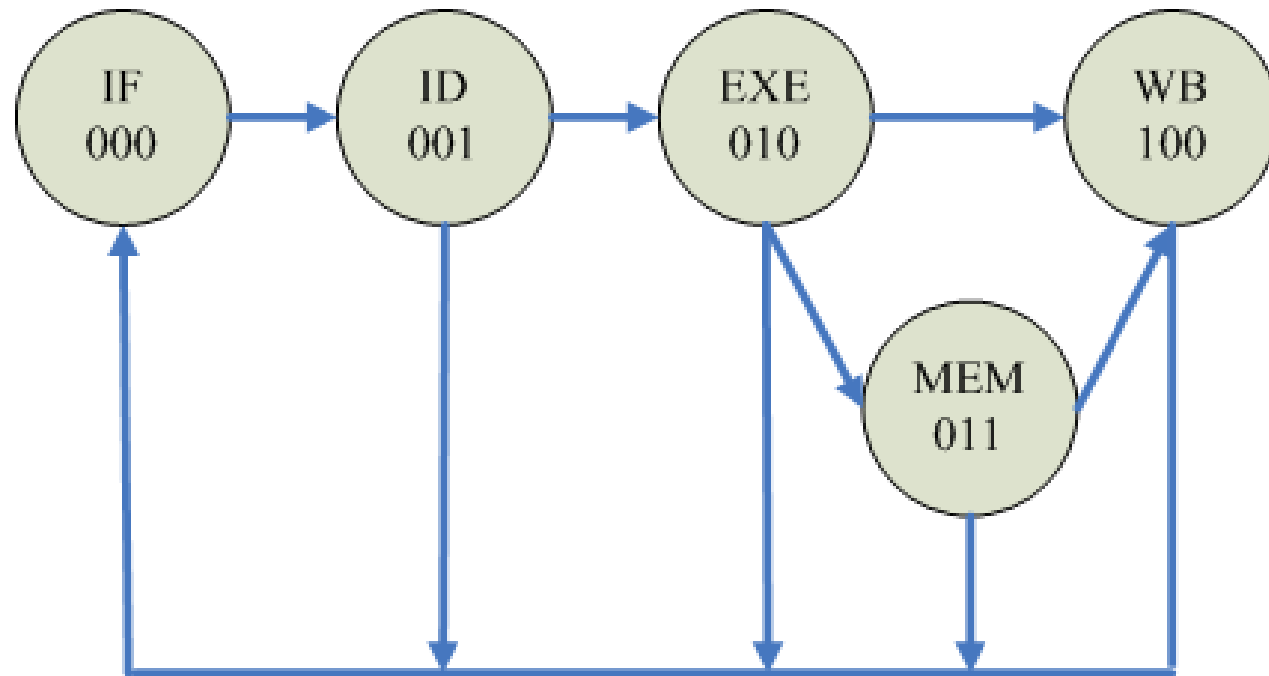


Stages of Multiple-Cycle Execution of Typical MIPS CPU

The principle of CPU Controller(2)

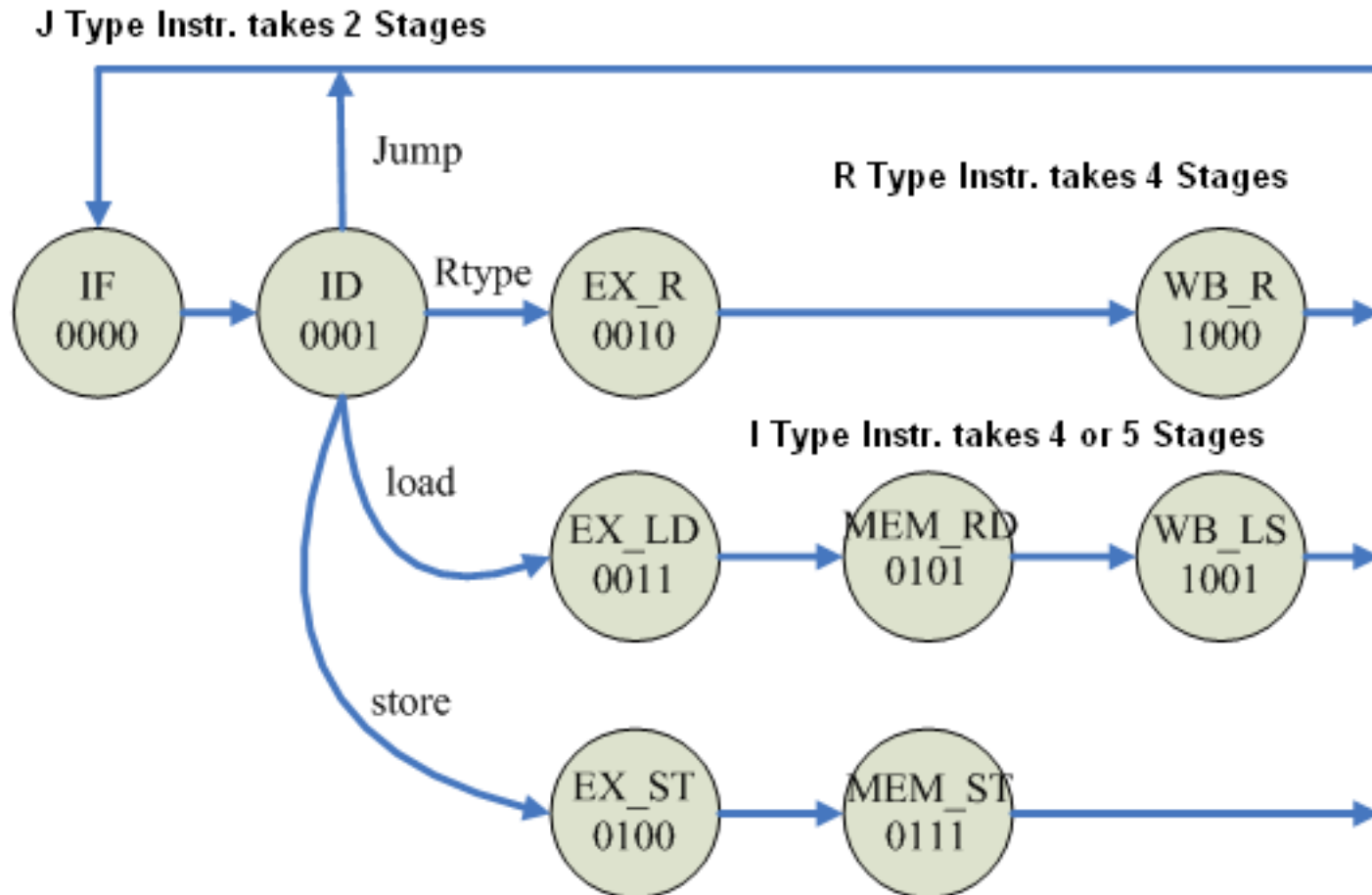

Multiple Cycle CPU Stages State Machine

The Datapath of Multiple-cycle CPU

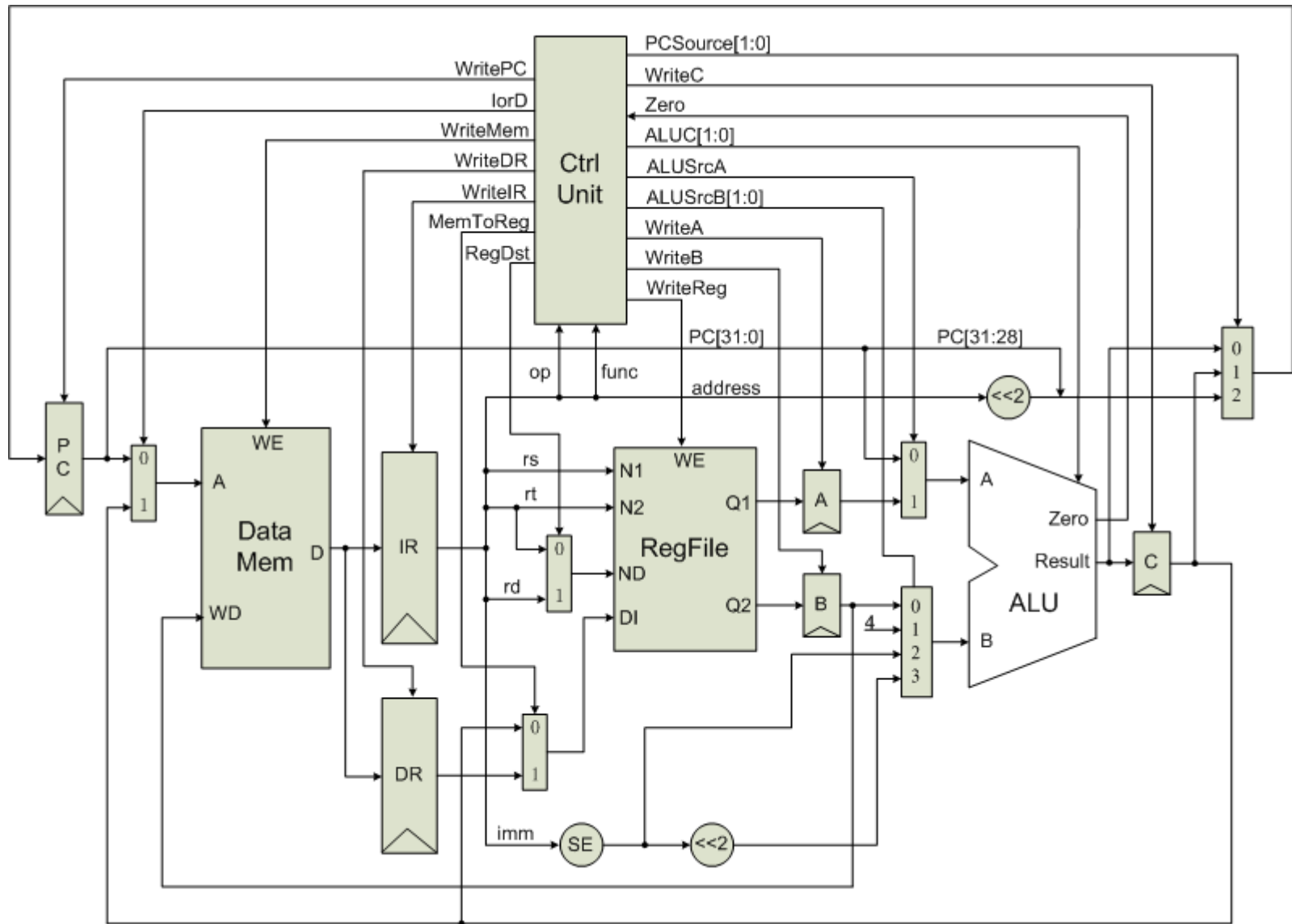

Basic Units of Multiple-cycle CPU

- CPU Controller
- ALU and ALU Controller
- Register file
- Mem. (Instruction and Data together).
- others: Register, sign-extend Unit, shifter, multiplexor

Memory

- Memory
 - Dual Port Block Memory
 - Port A: Read Only, Width: 32, Depth: 512
 - Port B: Read and Write, Read After Write
 - Rising Edge Triggered

Multiple-cycle CPU Top Module

- memory
x_memory(.addra(raddr),.addrb(waddr),.clka(clk), .clkb(clk),.dinb(b_data),
.douta(mem_data),.web(write_mem));
- ctrl x_ctrl(clk, rst, ir_data, zero,write_pc, iord, write_mem, write_dr,
write_ir, memtoreg, regdst, pcsource, write_c, alu_ctrl, alu_srcA,
alu_srcB, write_a, write_b, write_reg, state_out, insn_type, insn_code,
insn_stage);
- pcm x_pcm(clk, rst, alu_out, c_data, ir_data, pcsource, write_pc,pc);
- alu_wrapper x_alu_wrapper(a_data, b_data, ir_data, pc, alu_srcA,
alu_srcB, alu_ctrl, zero, alu_out);
- reg_wrapper x_reg_wrapper(clk, rst, ir_data, dr_data, c_data, memtoreg,
regdst, write_reg, rdata_A, rdata_B, r6out);

Observation Info

■ Input

- West Button: Step execute
- South Button: Reset
- Slide Button: Address of Register

■ Output

- 0-7 Character of First line: Instruction Code
- 8 of First line : Space
- 9-10 of First line : Read Address
- 11 of First line : Space
- 12-13 of First line : Write Address
- 0/2/4/6 of Second line : state/type/code/**stage**
- 8-9 of Second line : PC
- 11-14 of Second line: Selected Register Content

Program for verification


- <0> lw r1, \$20(r0); 0x8c01_0014 State:0,1,3,5,9 Type:3 Code:1 (LD)
 - <1> lw r2, \$21(r0); 0x8c02_0015 State:0,1,3,5,9 Type:3 Code:1 (LD)
 - <2> add r3, r1, r2; 0x0022_1820 State:0,1,2,8 Type:1 Code:3 (AD)
 - <3> sub r4, r1, r2; 0x0022_2022 State:0,1,2,8 Type:1 Code:4 (SU)
 - <4> and r5, r3, r4; 0x0064_2824 State:0,1,2,8 Type:1 Code:5 (AN)
 - <5> nor r6, r4, r5; 0x0085_3027 State:0,1,2,8 Type:1 Code: 6 (NO)
 - <6> sw r6, \$22(r0); 0x ac06_0016 State:0,1,4,7 Type:3 Code: 2 (ST)
 - <7> J 0; 0x0800_0000 State:0,1 Type:2 Code:7 (JP)
-
- DataMem(20) = 0xbeef_0000 ;
 - DataMem(21) =0x0000_beef ;

Precaution


- 1. Add Anti-Jitter
- 2. Finish the State Machine
- 3. Add Stage Status

Step2 Comparison of three CPUs' work


Simple-Cycle CPU

 


Multiple-Cycle CPU

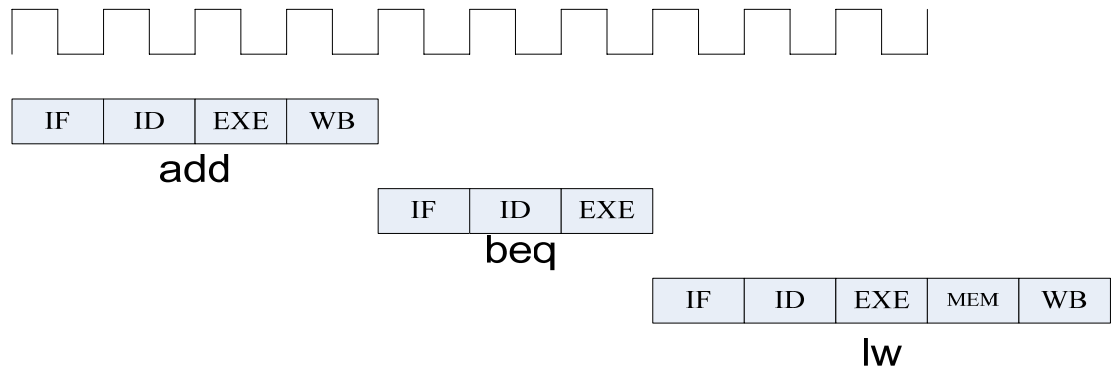


Pipelined CPU

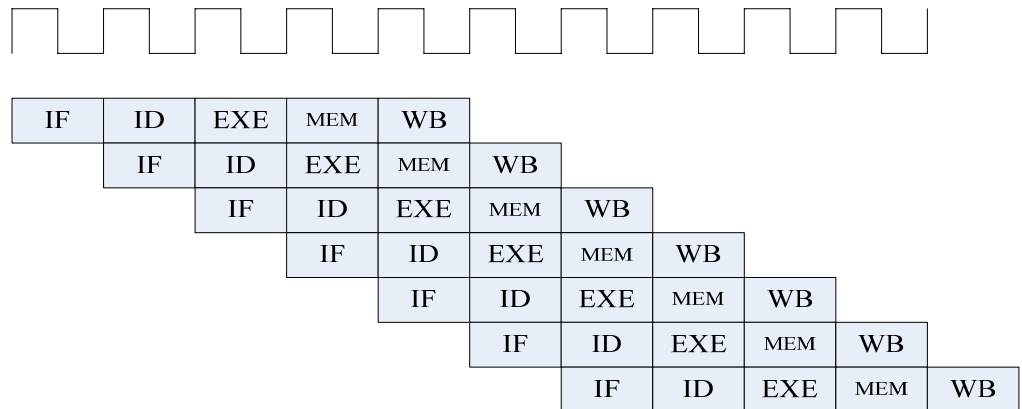

Datapath of 5-stages Pipelined CPU

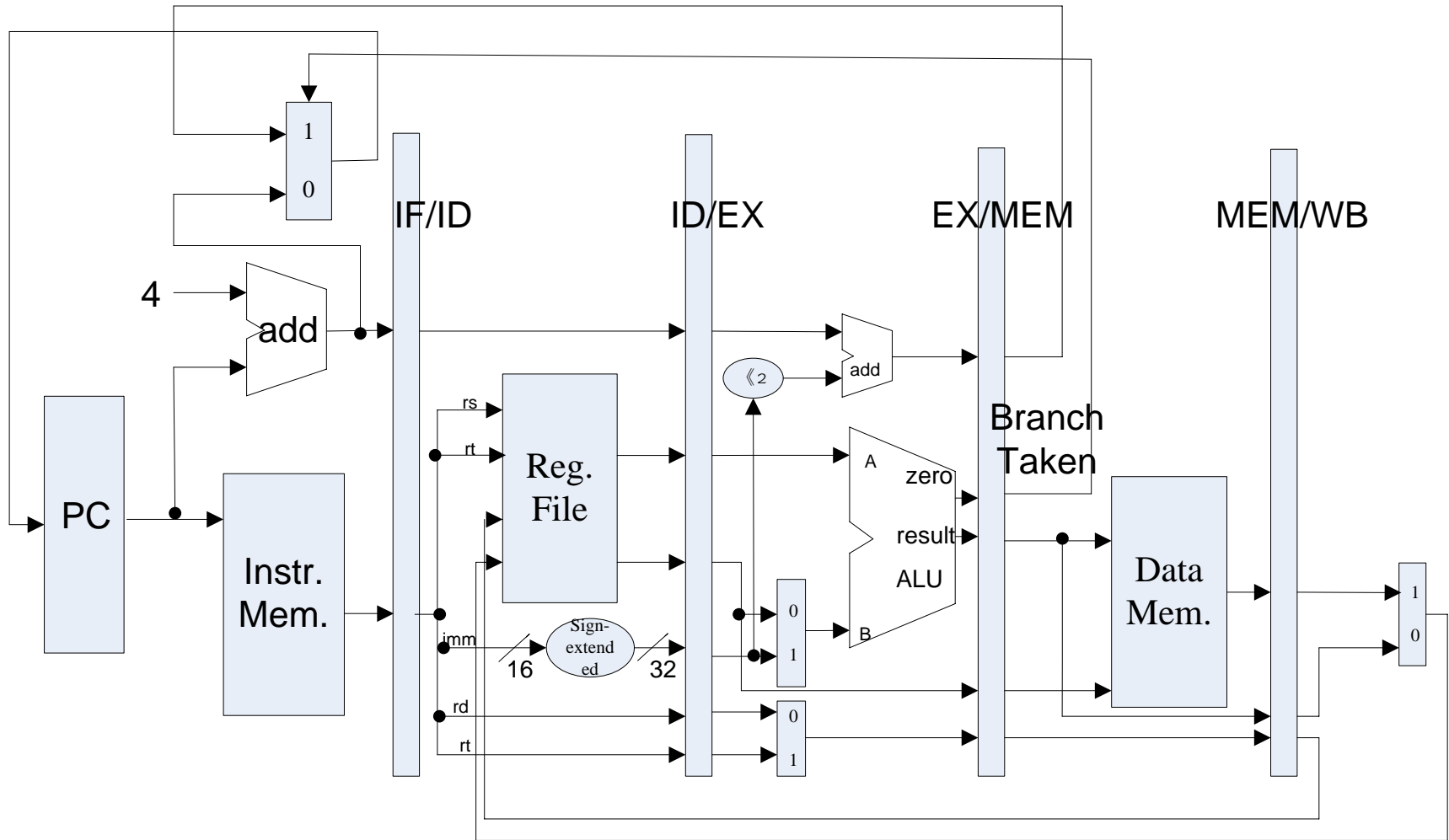


The principle of Multiple-cycle CPU

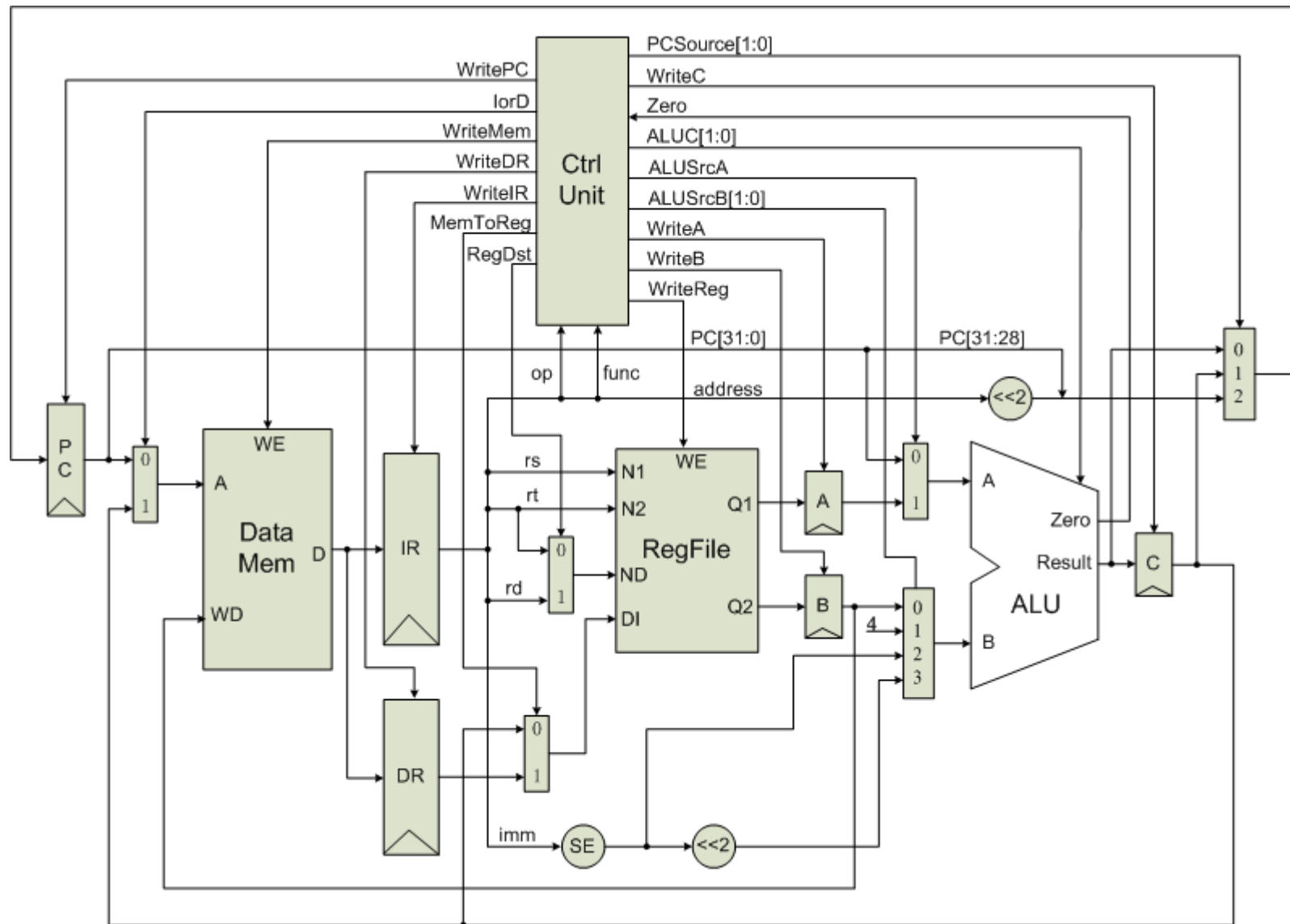

Structural hazards — resource conflicts

- Structural hazards arise from resource conflicts when the hardware cannot support all possible combinations of instructions in simultaneous overlapped execution.
 - Memory conflicts
 - Register File conflicts
 - Other units conflicts

How to resolve Structural hazards

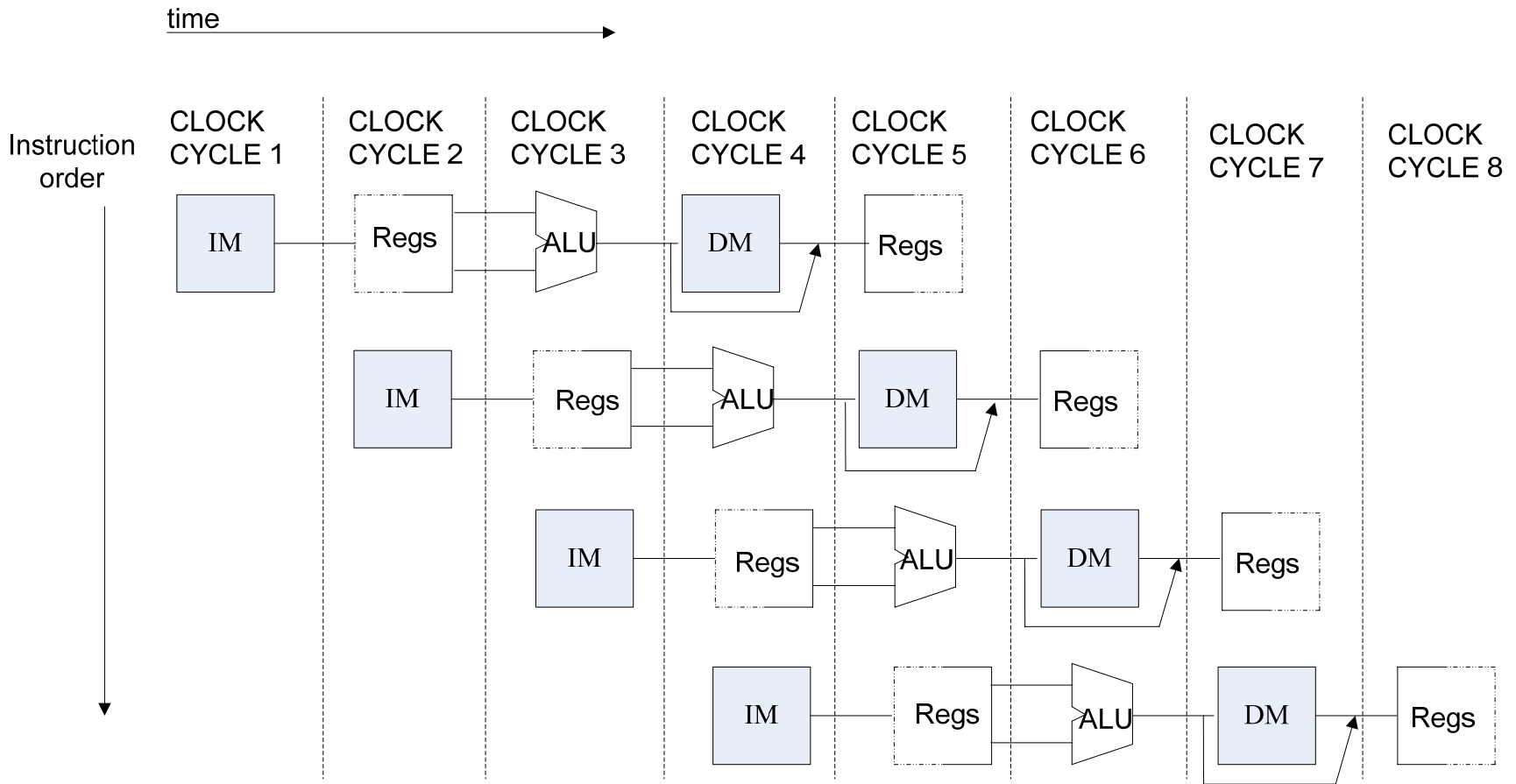

Register File


- Register File

- Positive edge for transfer data for stages
- Negative edge for write operation
- Low level for read operation

Memory

- Instruction Memory
 - Single Port Block Memory
 - Read only, Width:32
 - Falling Edge Triggered
- Data Memory
 - Single Port Block Memory
 - Read and write, Width:32
 - Falling Edge Triggered

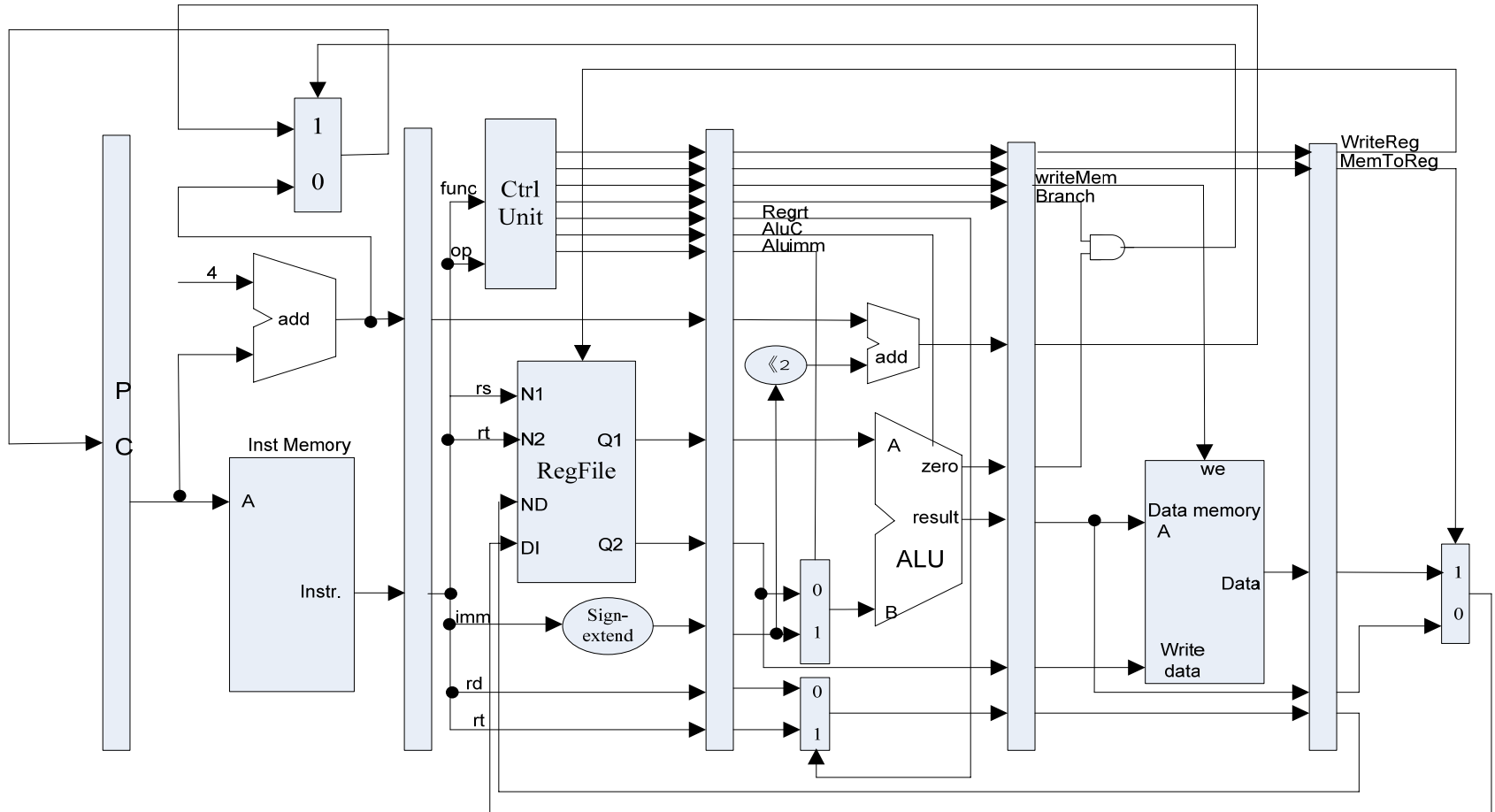The principle of Pipelined CPU—with CPU controller




Output of CPU Controller

	Output Signal	Meaning When 1	Meaning When 0
1	Cu_branch	Branch Instr.	Non-Branch Instr.
2	Cu_shift	sa	Register data1
3	Cu_wmem	Write Mem.	Not Write Mem.
4	Cu_Mem2Reg	From Mem. To Reg	From ALUOut To Reg
5	Cu_sext	Sign-extend the imm.	No sign extended the imm.
6	Cu_aluc	ALU Operation	
7	Cu_aluimm	Imm.	Register data2
8	Cu_wreg	Write Reg.	Not Write Reg.
9	Cu_regrt	rt	rd

Units of Pipelined-cycle CPU

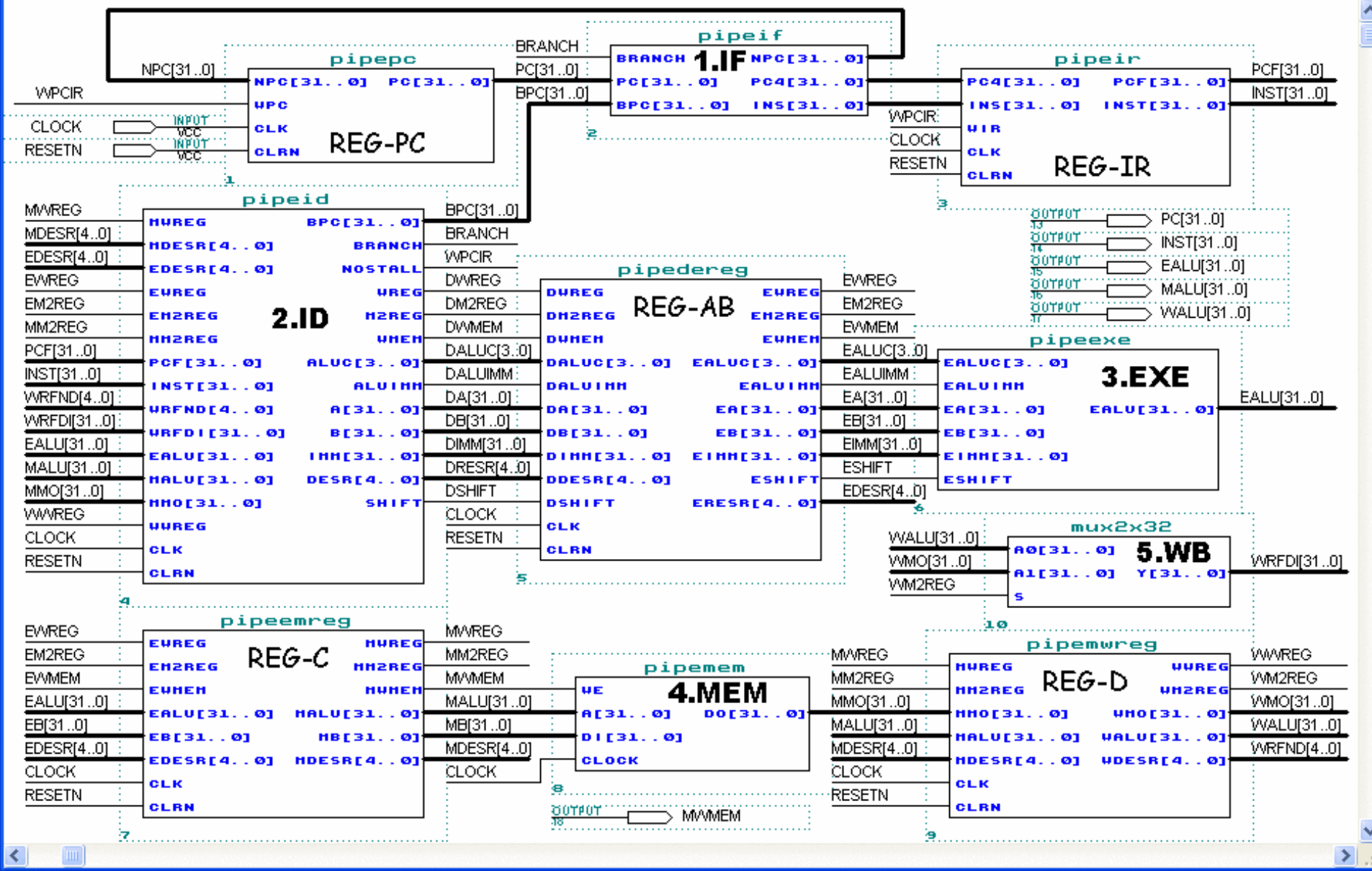- IF Stage (Instr. Mem.)
- ID Stage (CPU Ctl. And R.F.)
- EX Stage (ALU)
- Mem Stage (Data Mem.)
- WB Stage



Pipelined CPU Top Module

- module top (input wire CCLK, BTN3, BTN2, input wire [3:0]SW, output wire LED, LCDE, LCDRS, LCDRW, output wire [3:0]LCDDAT);
-
- assign pc [31:0] = if_npc[31:0];
-
- if_stage x_if_stage(BTN3, rst, pc, mem_pc, mem_branch, ...
- IF_ins_type, IF_ins_number, ID_ins_type, ID_ins_number);
-
- id_stage x_id_stage(BTN3, rst, if_inst, if_pc4, wb_destR, ...
- ID_ins_type, ID_ins_number, EX_ins_type, EX_ins_number..);
-
- ex_stage x_ex_stage(BTN3, id_imm, id_inA, id_inB, id_wreg, ..
- EX_ins_type, EX_ins_number, MEM_ins_type, MEM_ins_number);
-
- mem_stage x_mem_stage(BTN3, ex_destR, ex_inB, ex_aluR, ...
- MEM_ins_type, MEM_ins_number, WB_ins_type, WB_ins_number);
-
- wb_stage x_wb_stage(BTN3, mem_destR, mem_aluR, ...
- WB_ins_type, WB_ins_number, OUT_ins_type, OUT_ins_number);

Observation Info

■ Input

- West Button: Step execute
- South Button: Reset
- 4 Slide Button: Register Index

■ Output

- 0-7 Character of First line: Instruction Code
- 8 of First line : Space
- 9-10 of First line : Clock Count
- 11 of First line : Space
- 12-15 of First line : Register Content
- Second line : “stage name”/number/type
- stage name: 1-“f”, 2-“d”, 3-“e”, 4-“m”, 5-“w”

Program for verification

	Instruction	Bin Code	Address	Inst. Type
1	lw r1, \$20(r0)	0x8c01_0014	0	6
2	lw r6, \$21(r0)	0x8c06_0015	1	6
3	add r3,r0,r0	0x0000_1820	2	1
4	add r4,r0,r0	0x0000_2020	3	1
5	add r5,r0,r0	0x0000_2820	4	1
6	add r2,r2,r1	0x0041_1020	5	1
7	sub r3, r3, r1	0x0061_1822	6	2
8	and r4, r4, r1	0x0081_2024	7	3
9	nor r5, r5, r1	0x00a1_2827	8	5
10	beq r2, r1, -8	0x1041_fff8	9	8

Precaution

- 1. Add Anti-Jitter and display for “A-F”.
- 2. Finish the blank.
- 3. Debug method: Output whatever signal to LCD Display.
- 4. Understand the principle of pipelined CPU and check the logic of circuit carefully, understand the sample code, then write code and synthesize the project, because it takes you a few minutes...

Something Important !!!

- 1、 The number and type tells the information of the instruction that is to be executed in the stage.
- 2、 How to verify the result? Pls. check the result of WB stage for R-type and LW instructions, while check the result of EXEC stage for BEQ instruction.
- 3、 Why there are some NONE instructions following BEQ? How many NONE instructions? 3, because the condition of BEQ is generated in MEM stage.
- 4、 Why the initial value of PC is FFFFFFFF, not 0?
- 5、 Why we should pull the slide button after step execution to refresh the result? And instruction refresh is delayed by 1 clock-cycle? How to refresh automatically?

■ Thanks!